

HOUR TEST #3

.....
HONOR PLEDGE:

In completing this test, I have neither given nor received unauthorized assistance.

(signature)
.....

- This is a closed-book, closed-notes test. No written material is allowed.
- You are permitted to use an electronic calculator only to assist with numerical work.
- Assume that the given quantities are accurate enough to justify three (and only three) figures in your final answers.
- **Show your work, especially on the problems!** Credit, especially partial credit on problems where your final answer is incorrect, will depend on the work shown.

The test consists of 15 questions and 2 problems. Perfect score is 100.

Questions 1-15 count 4 points each. (60%)

Problems 1-2 count 20 points each. (40%)

Possibly useful information.

terrestrial acceleration due to gravity:	$g = 9.80 \text{ m/s}^2$	
π	3.14159265	$e = 2.71828183$
1 eV	$= 1.602 \times 10^{-19} \text{ J}$	$\log_{10} e = 0.43429448$
1 year	$= 3.156 \times 10^7 \text{ sec}$	
astronomical unit (AU)	$= 1.496 \times 10^{11} \text{ m}$	
speed of light in vacuum:	$c = 2.998 \times 10^8 \text{ m/s}$	
constant of gravitation:	$G = 6.673 \times 10^{-11} \text{ N}\cdot\text{m}^2/\text{kg}^2$	
Planck's constant:	$h = 6.626 \times 10^{-34} \text{ J}\cdot\text{s} = 4.136 \times 10^{-15} \text{ eV}\cdot\text{s}$	
"h-bar"	$\hbar \equiv h/2\pi = 1.055 \times 10^{-34} \text{ J}\cdot\text{s} = 6.583 \times 10^{-16} \text{ eV}\cdot\text{s}$	
Boltzmann constant:	$k = 1.381 \times 10^{-23} \text{ J/K} = 8.617 \times 10^{-5} \text{ eV/K}$	
Avogadro's number	$N_A = 6.022 \times 10^{23} \text{ particles/mole}$	
Universal gas constant:	$R = N_A k = 8.315 \text{ J/(mol}\cdot\text{K)}$	
Stefan-Boltzmann constant:	$\sigma = 5.671 \times 10^{-8} \text{ W/(m}^2\text{K}^4)$	
unified mass unit (dalton):	$(1 \text{ u}) = 1.661 \times 10^{-27} \text{ kg}$	
energy equivalent of 1 dalton:	$(1 \text{ u})c^2 = 1.493 \times 10^{-10} \text{ J} = 931.9 \text{ MeV}$	
proton (rest) mass:	$m_p = 1.673 \times 10^{-27} \text{ kg}$	
rest energy of proton:	$m_p c^2 = 1.504 \times 10^{-10} \text{ J} = 938.6 \text{ MeV}$	
electron (rest) mass:	$m_e = 9.109 \times 10^{-31} \text{ kg}$	
rest energy of electron:	$m_e c^2 = 9.187 \times 10^{-14} \text{ J} = 0.5111 \text{ MeV}$	
elementary unit of charge:	$e = 1.602 \times 10^{-19} \text{ C}$	
product of h and c:	$hc = 1.987 \times 10^{-25} \text{ J}\cdot\text{m} = 1.240 \times 10^{-6} \text{ eV}\cdot\text{m} = 1240 \text{ eV}\cdot\text{nm}$	
standard temperature:	$T = 0^\circ\text{C} = 273.15 \text{ K}$	
standard pressure:	$P = 1.000 \text{ atmosphere} = 1.013 \times 10^5 \text{ N/m}^2$	

Questions 1-15. (4 points each) On most of these questions, partial credit is not available. You are not required to show your work.

Q1. The electrostatic field just outside the surface of a conductor _____.

- (A) is always zero
- (B) is always parallel to the surface
- (C) is always perpendicular to the surface
- (D) cannot be directed outward if the overall charge on the conductor is zero

Q1. C

Q2. The SI unit for electric field can be written as 1 N/C (one newton per coulomb). This is equivalent to _____.

- (A) 1 V/m²
- (B) 1 V/m
- (C) 1 V
- (D) 1 V·m
- (E) 1 V·m²

Q2. B

Q3. Write a correct SI unit for electric dipole moment.

Q3. C·m or Coulomb-meters

Q4. How much electrostatic potential energy is stored when an initially "uncharged" 5.00-microfarad capacitor is "charged up" to a potential difference of 30.0 volts?

$$P.E. = \frac{1}{2} C V^2 = \frac{1}{2} (5 \times 10^{-6}) (30.0)^2 = 2.25 \times 10^{-3}$$

Q4. $2.25 \times 10^{-3} \text{ J}$

Q5. The magnitude of the electric field above a uniformly charged infinite horizontal sheet _____ the distance above the sheet.

- (A) varies in direct proportion to
- (B) varies in inverse proportion to
- (C) varies directly as the square of
- (D) varies inversely as the square of
- (E) is independent of
- (F) varies directly as the logarithm of
- (G) varies inversely as the logarithm of

Q5. E

Q6. Two capacitors ($C_1 = 8.00 \mu\text{F}$ and $C_2 = 6.00 \mu\text{F}$) are connected in series in a circuit. What is the effective capacitance of this combination? Include correct units for your answer.

$$C_{\text{series}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{48}{14} \mu\text{F} = 3.43 \mu\text{F}$$

Q6. $3.43 \mu\text{F}$

Q7-8. A constant potential difference V_0 is applied to a cylindrical resistor that has cross-sectional area A and total resistance R .

Q7. Write an expression for the power delivered to the resistor in terms of given quantities.

$$\text{DC Power} = V_0 I = V_0 \left(\frac{V_0}{R} \right)$$

Q7. V_0^2/R

Q8. Write an expression for the current density j in the resistor in terms of given quantities.

$$j = \frac{I}{A} = \frac{V_0}{AR}$$

Q8. V_0/AR

Q9. Carefully state Kirchhoff's current law (KCL).

Q9. The sum of the currents leaving any node is zero.

Q10. A capacitor ($C = 25.0 \times 10^{-6} \text{ F}$) is initially "charged" to a potential difference of 50.0 volts. Then, beginning at time zero, the capacitor is "discharged" through a resistor of resistance R . The potential difference across the capacitor is found to vary with time

according to $V_C(t) = (50.0 \text{ volts})e^{-\frac{t}{(0.200 \text{ sec})}}$. What is the value of the resistance?

Include proper units.

$$RC = 0.200 \text{ sec} \Rightarrow R = \frac{0.200 \text{ sec}}{25.0 \times 10^{-6} \text{ F}} = 8000 \Omega$$

Q10. 8000Ω

Q11. $\oint_{\text{closed surface}} \vec{B} \cdot d\vec{S} =$

(A) 0

(B) $Q_{\text{net}}/\epsilon_0$

(C) $\mu_0 I_{\text{conduction}}$

(D) $\mu_0 I_{\text{displacement}}$

(E) $\mu_0 (I_{\text{conduction}} + I_{\text{displacement}})$

Q11. A

Q12. (True or False) In a propagating electromagnetic wave in vacuum, the electric field is always perpendicular to the magnetic field and one of the two fields is always parallel to the direction of propagation. X

Q12. False

Q13. Which of the following is **NOT** the correct form of one of Maxwell's equations in differential form?

(A) $\vec{\nabla} \cdot \vec{E} = \frac{\rho}{\epsilon_0}$

(B) $\vec{\nabla} \cdot \vec{B} = 0$

(C) $\vec{\nabla} \times \vec{B} = \mu_0 \vec{J} + \mu_0 \epsilon_0 \frac{\partial \vec{E}}{\partial t}$

(D) $\vec{\nabla} \times \vec{E} = \mu_0 \epsilon_0 \frac{\partial \vec{B}}{\partial t}$

Q13. D


Q14. Express the complex number $z = -6.00 + i(4.00)$ in exponential form:

$$|z| = \sqrt{(-6)^2 + 4^2} = \sqrt{52} = 7.21$$


$$\theta = \tan^{-1}\left(\frac{4}{-6}\right) + \pi = -0.588 + 3.142 = 2.554 \text{ rad}$$

Q14. $\sqrt{52} e^{i(2.55)}$

Q15. Draw and label a simple circuit that can be used as a high-pass filter.

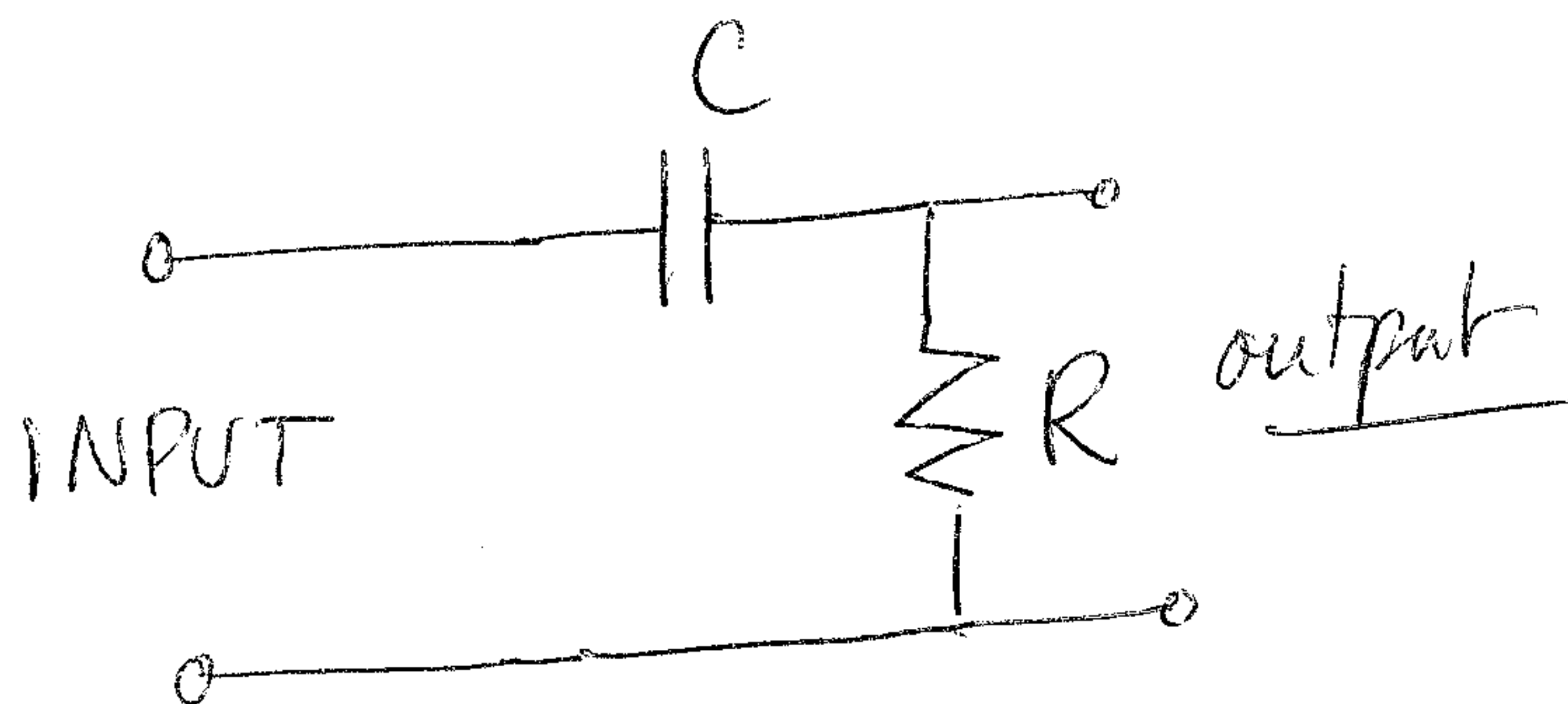

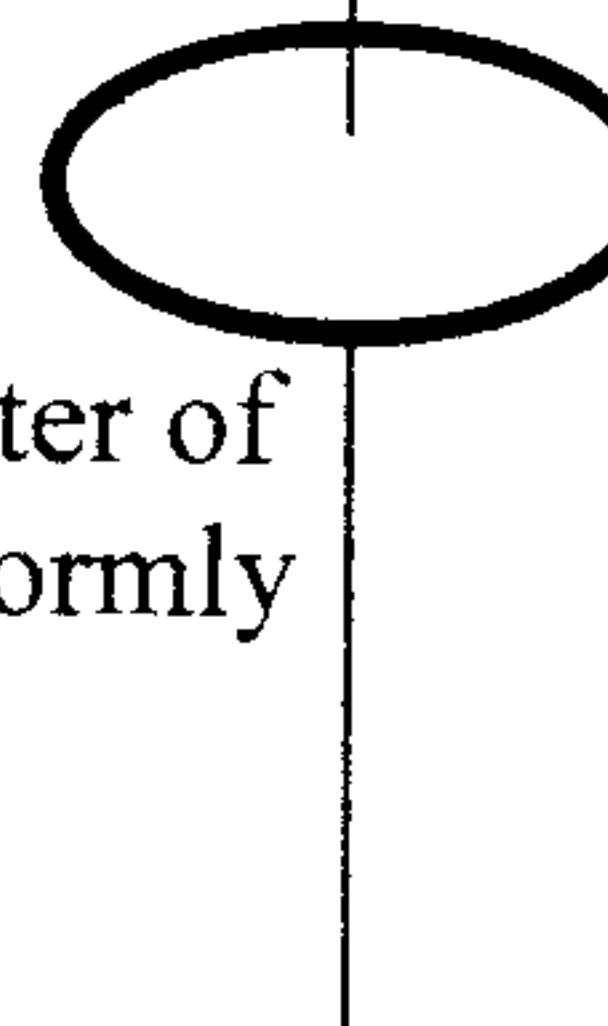Problem 1. (20 points) Show your work. Partial credit will depend on that.



Consider a circular ring of positive charge. The ring lies in the xy plane and the center of the ring is at the origin. The radius of the ring is b , and the total charge $Q > 0$ is uniformly distributed on the ring. Express your answers below in terms of Q , b , and physical constants.

(A) Determine λ , the charge per unit length on the ring.

$$\lambda = \frac{Q}{2\pi b}$$

(B) Using the usual convention that the electrostatic potential is zero at great (infinite) distance from the origin, what is the electrostatic potential V_{origin} at the center of the ring? Justify your answer.

Since all of the charge is at the same distance (b) from the origin,

$$V_{\text{origin}} = \frac{1}{4\pi\epsilon_0} \sum_i \frac{dq_i}{r_i} = \frac{Q}{4\pi\epsilon_0 b}$$

(C) Determine the electrostatic potential as a function of z along the z axis: $V(0,0,z) = ?$ Justify your answer.

Again, all parts of the ring are at the same distance ($\sqrt{b^2 + z^2}$) from the point $(0,0,z)$.

$$V(0,0,z) = \frac{Q}{4\pi\epsilon_0 \sqrt{b^2 + z^2}}$$

(Problem 1 continues on the next page.)

5) **Problem 1. (continued)**

(D) Use your answer to part (C) to determine the electric field $\mathbf{E}(\mathbf{r})$ for $\vec{r} = 0\hat{i} + 0\hat{j} + 3b\hat{k}$. Show your work and be sure to express the electric field as a vector.

$$\vec{E} = -\vec{\nabla} V$$

By symmetry, $\vec{E}$ has only a z component (as long as we stay on the z axis).


$$\text{So } \vec{E} = -\hat{k} \frac{\partial V}{\partial z} = -\hat{k} \left(\frac{Q}{4\pi\epsilon_0} \right) \frac{\partial}{\partial z} \left((b^2 + z^2)^{-1/2} \right)$$

$$= -\hat{k} \frac{Q}{4\pi\epsilon_0} \left[-\frac{1}{2} \frac{(2z)}{(b^2 + z^2)^{3/2}} \right] = \hat{k} \frac{Q}{4\pi\epsilon_0} \frac{z}{(b^2 + z^2)^{3/2}}$$

For $z = 3b$, get

$$\underline{\underline{\vec{E}}} = \hat{k} \frac{Q}{4\pi\epsilon_0} \frac{3b}{(10b^2)^{3/2}} = \underline{\underline{\hat{k} \frac{3}{10\sqrt{10}} \left(\frac{Q}{4\pi\epsilon_0 b^2} \right)}}$$

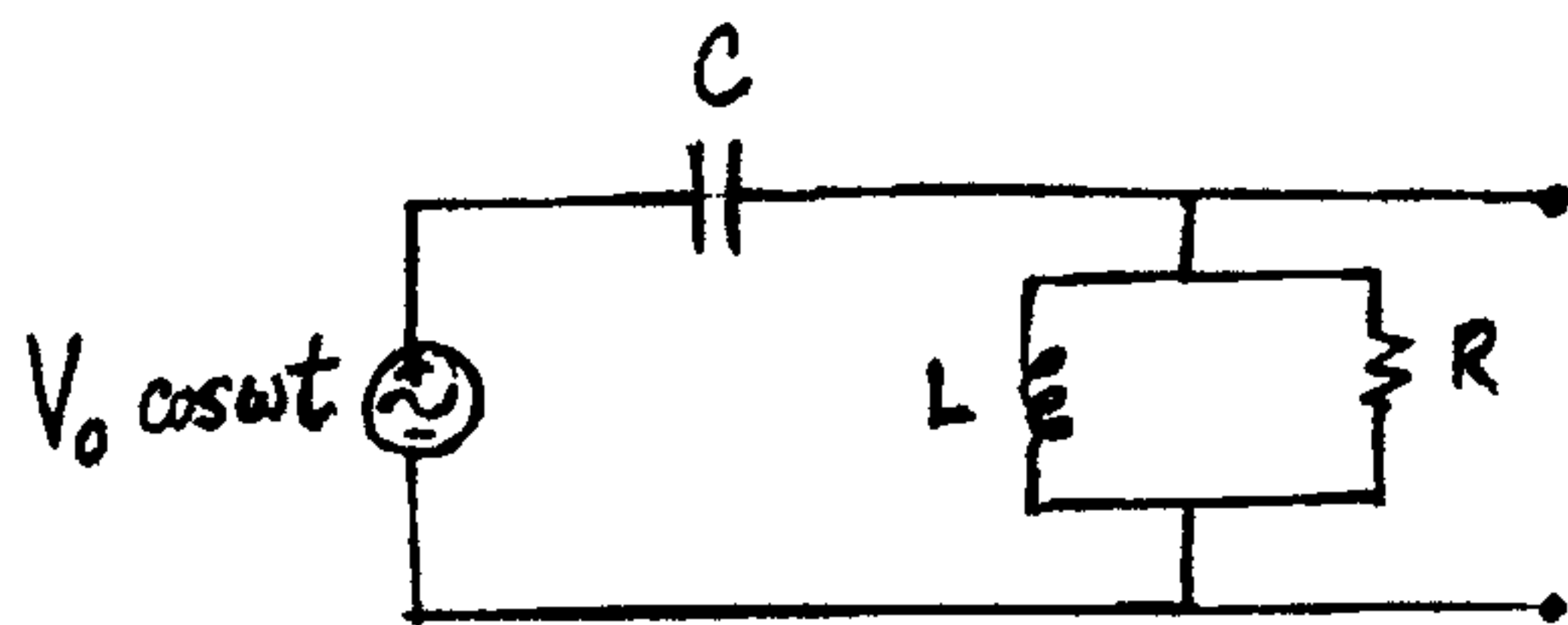Problem 2. (20 points) Show your work. Partial credit will depend on that.



Consider the electric circuit shown above. Note that this is NOT a series RLC circuit! Give your answers for (A)-(C) below in terms of V_0 , ω , C , L , and R and any necessary mathematical constants.

(A) What is the (complex) impedance Z_C of the capacitor? (Express it in rectangular form.)

$$\underline{Z_C} = -iX_C = -\frac{i}{\omega C} = \underline{0 - i\left(\frac{1}{\omega C}\right)}$$

(B) Determine the (complex) impedance Z_2 of the parallel LR combination. (Express your result in rectangular form.)

$$\underline{Z_2} = \frac{Z_L Z_R}{Z_L + Z_R} = \frac{(i\omega L)R}{i\omega L + R}$$

$$\underline{Z_2} = \frac{i\omega LR(R - i\omega L)}{R^2 + (\omega L)^2} = \underline{\underline{\frac{R(\omega L)^2}{R^2 + (\omega L)^2} + \frac{i(\omega L)R^2}{R^2 + (\omega L)^2}}}$$

(C) Show that the (complex) impedance Z_{final} of the series combination of the capacitor

and the LR (parallel) combination is given by $Z_{\text{final}} = \frac{(\omega L)^2 R}{R^2 + (\omega L)^2} + i \left[\frac{(\omega L)R^2}{R^2 + (\omega L)^2} - \frac{1}{\omega C} \right]$

Series combination $\Rightarrow$

$$\underline{Z_{\text{final}}} = \underline{Z_C + Z_2} = \underline{\underline{\frac{(\omega L)^2 R}{R^2 + (\omega L)^2} + i \left[\frac{(\omega L)R^2}{R^2 + (\omega L)^2} - \frac{1}{\omega C} \right]}}$$

(Problem 2 continues on the next page.)

Problem 2. (continued)

5) (D) If the sinusoidal voltage source is represented by the phasor $\mathbf{V}_0 = V_0 e^{i\omega t}$ and the (rightward) current through the capacitor is represented by the phasor $\mathbf{I}_0 = I_0 e^{i(\omega t + \phi)}$, describe how to determine the magnitude I_0 and phase constant ϕ of the current phasor. You do not need to actually determine their values.

$$\mathbf{V}_0 = V_0 e^{i\omega t} = \mathbf{I}_0 Z_{\text{final}}, \text{ so}$$

$$I_0 e^{i(\omega t + \phi)} = \frac{V_0 e^{i\omega t}}{Z_{\text{final}}}$$

That is, find the current phasor $\mathbf{I}_0$ by dividing the voltage phasor $\mathbf{V}_0$ by the complex impedance Z_{final} . Obtaining $I_0 + \phi$ will be easiest if Z_{final} is re-expressed in exponential form.